

ABE 460

Lab Week 7: Process Identification and Empirical Modeling

Kathryn Atherton

October 1, 2018

Monday

## Problem 3.1

a) First order time function =  $y(t) = y_{ss} + (y_0 - y_{ss})e^{-t/\tau}$

$$Y_{ss} = 80$$

$$Y_0 = 256$$


From MATLAB:  $\tau = 17$  seconds

$$\text{Overall time function} = y(t) = 80 + (256 - 80)e^{-t/17s}$$

$$\text{First order transfer function} = \frac{1}{\tau s + 1}$$


$$\text{Overall transfer function} = \frac{1}{17s + 1}$$

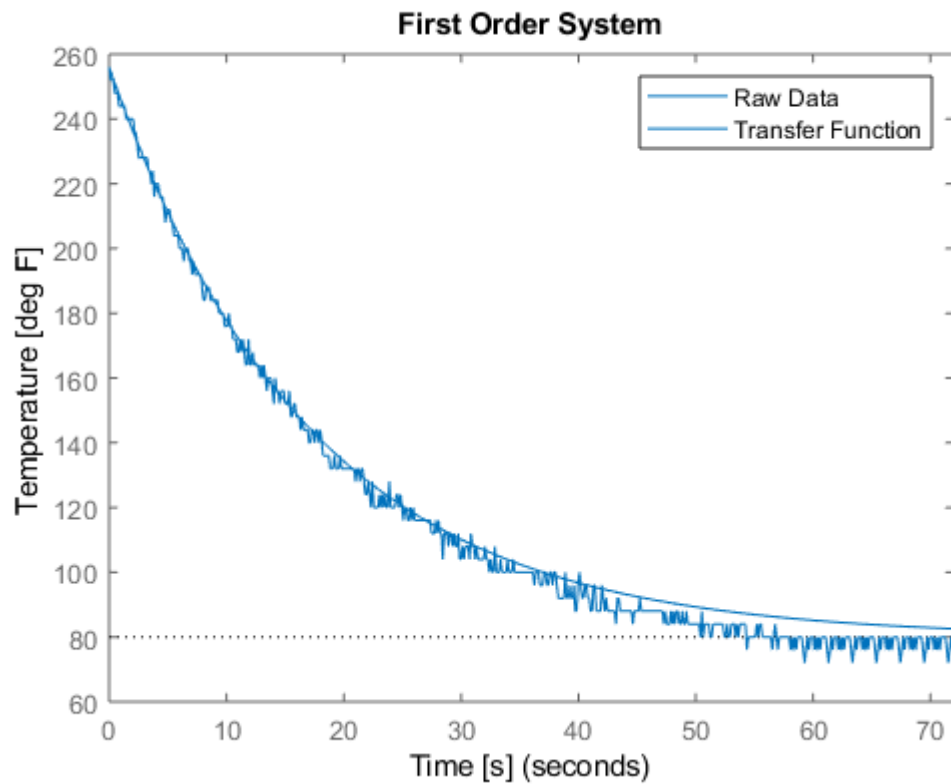b) Output variable = temperature (degrees F)



c)


*Figure 1: First Order System Raw Data and Transfer Function Plot*

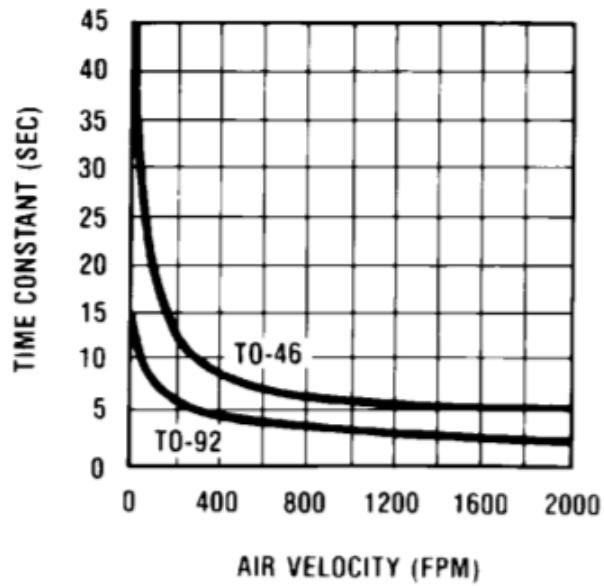

d)

*Figure 3: Time constant comparison for T0-92 Model*

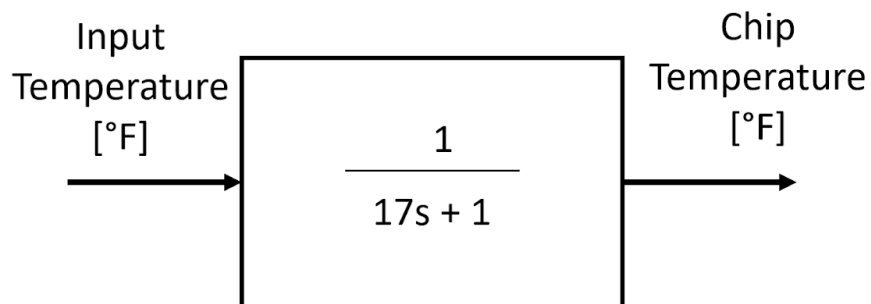According to Figure 3, the published time constant is about 15 seconds when the air velocity is 0 fpm. This is an 11% error.



e)

*Figure 4: First Order Transfer Function Block Diagram*

```

chip_temp = IC_chip;
chip_time = 0:0.12:72;
time_constant = 16.8;
output_exp = chip_temp ./ 10;

y_ss = 80;
y0 = 256;

num = [1];
den = [time_constant 1];
sys = tf(num, den);
stepOpts = stepDataOptions('InputOffset', y0, 'StepAmplitude', y_ss-y0);
step(sys, 72, stepOpts);

figure(1)
hold on
plot(chip_time, output_exp, '--')
axis([0 80 0 300])
xlabel('Time (sec)')
ylabel('Temp (F)')
legend('Experiment')

```

Figure 5: MATLAB Code for Problem 3.1

### Problem 3.2

a)  $V_{in} - V_R - V_L - V_C = 0$

$$V_{in} - Ri - L \frac{di}{dt} - \frac{1}{C} \int i dt = 0$$

$$i = \frac{dq}{dt}$$

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V_{in}$$

$$V_C = \frac{1}{C} \int i dt = \frac{q}{C}$$

$$LC \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C = V_{in}$$

b) Zeta = 0.55680

Peak time = 31.84

Natural frequency = 0.1188

$$c(t) = 1 - \frac{e^{-0.55680-0.1188t}}{\sqrt{1-0.55680^2}} \cdot \sin(0.1188\sqrt{1-0.55680^2}t + \tan^{-1}\frac{\sqrt{1-0.55680^2}}{0.55680})$$

$$c(t) = 1 - \frac{e^{-0.006615t}}{0.8306} \cdot \sin(0.09868t + 0.9037)$$

$$TF = \frac{0.01411}{s^2 + 0.1323s + 0.01411}$$

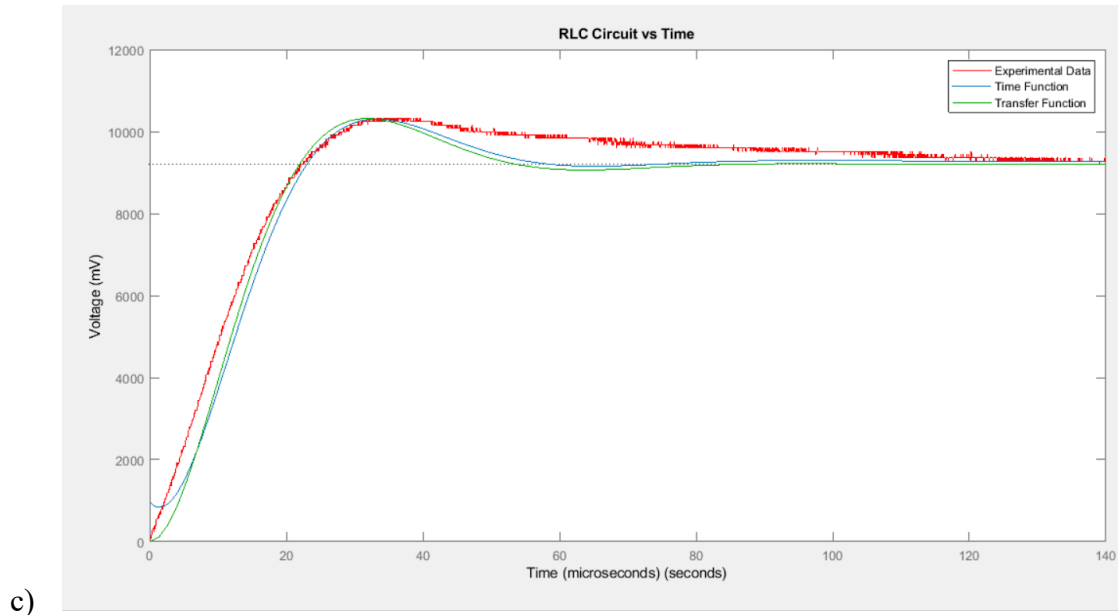


Figure 6: Second Order System Raw Data, Time Function, and Transfer Function Plots

d)  $C = 1\mu\text{F}$

$$1 = \frac{1}{LC}$$

$$1 = \frac{1}{L \cdot 1}$$

$$L = 1\mu\text{F}^{-1}$$

$$0.1323 = \frac{RC}{LC} = \frac{R}{L}$$

$$R = 0.1323 \mu\text{F}$$

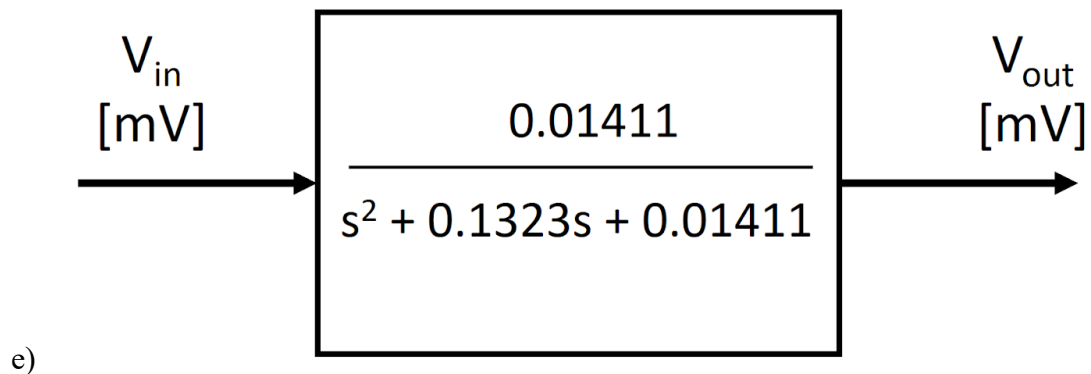


Figure 7: Second Order Transfer Function Block Diagram

```

circuit_time = 0:0.04:140; %Time matrix
output_volt = VC_output'; %Experimental data matrix of voltage values
peak_val = max(output_volt); %Peak value of Vc
zeta = 0.55680; %Damping ratio
peak_time = 31.84; %Time it takes to cross steady state value (9280) in us
natural_freq = 3.14159265 / peak_time / sqrt(1-zeta^2);
sq_nat_freq = natural_freq^2;
mid = 2*zeta*natural_freq;

top = [sq_nat_freq];
bottom = [1 mid sq_nat_freq];
system = tf(top, bottom);

figure(2)
plot(circuit_time,output_volt, 'r')
hold on
ezplot('9280*(1 - ((exp(-0.557*0.118804*x)/sqrt(1-0.557^2)) * sin(0.118804*sqrt(1-0.557^2)*x + atan(sqrt(1-0.557^2)/0.557))))')
stepOpts = stepDataOptions('InputOffset',0,'StepAmplitude',9200);
step(system, 140, stepOpts, 'g');
ylabel('Voltage (mV)')
xlabel('Time (microseconds)')
title('RLC Circuit vs Time')
legend('Experimental Data', 'Time Function', 'Transfer Function')

```

Figure 8: MATLAB Code for Problem 3.2